

---

# Experiments in Digital Technology

1st Edition

---

**© hps SystemTechnik**

Lehr- + Lernmittel GmbH  
Altdorfer Strasse 16  
88276 Berg (Germany)

Phone: +49 751/5 60 75 80  
Telefax: +49 751/5 60 75 17  
Internet: <http://www.hps-SystemTechnik.com>  
E-mail: [export@hps-SystemTechnik.com](mailto:export@hps-SystemTechnik.com)

**Order no.: V 0160**

All rights reserved. No part of this publication may be reproduced, transmitted, stored in a retrieval system, nor translated into any human or computer language, in any form or by any means, electronic, mechanical, magnetic, optical, chemical, manual or otherwise, without the prior permission of hps SystemTechnik.

## List of Contents

<b>Foreword</b> .....	1	<b>3. Bistable multivibrators</b> .....	29
<b>1. Basic logic circuits</b> .....	3	<b>3.1 Fundamental principles</b> .....	29
<b>1.1 Fundamental principles</b> .....	3	3.1.1 General .....	29
1.1.1 Forms of representation and aids .....	3	3.1.2 Asynchronous flipflops .....	29
1.1.2 Laws of switching algebra .....	5	3.1.3 Synchronous flipflops .....	31
1.1.3 Complete disjunctive normal form .....	6	<b>3.2 Experiments section</b> .....	33
1.1.4 Complete conjunctive normal form .....	6	3.2.1 RS flipflop consisting of NOR gates .....	33
1.1.5 KV diagrams .....	7	3.2.2 RS flipflop consisting of NAND gates ....	34
1.1.6 Logic functions with NOR and NAND elements .....	8	3.2.3 Clock state controlled RS flipflops .....	35
<b>1.2 Experiments section</b> .....	9	3.2.4 RS flipflops with dominant S or R input ...	36
1.2.1 Important binary logic operations .....	9	3.2.5 D flipflops .....	37
1.2.2 Laws of switching algebra .....	10	3.2.6 Single edge controlled RS flipflop .....	38
1.2.3 Disjunctive and conjunctive normal form ..	15	3.2.7 Two state controlled D flipflop .....	41
1.2.4 Circuit design with the aid of KV diagrams .....	17	3.2.8 Single edge controlled JK flipflop .....	42
1.2.5 Representation of switching networks in NAND and NOR technology .....	19	<b>4. Monostable multivibrators</b> .....	47
1.2.6 Equivalence .....	22	<b>4.1 Fundamental principles</b> .....	47
1.2.7 Antivalence .....	23	<b>4.2 Experiments section</b> .....	48
1.2.8 Working with TTL components .....	24	4.2.1 The monoflop of the Digital Training System .....	48
<b>2. Schmitt triggers</b> .....	27	4.2.2 Delay circuits .....	49
<b>2.1 Fundamental principles</b> .....	27	<b>5. Code converters, coders</b> .....	53
<b>2.2 Experiments section</b> .....	28	<b>5.1 Fundamental principles</b> .....	53
		5.1.1 General .....	53
		5.1.2 8421-BCD / three-excess code converter .	53

<b>5.2 Experiments section</b> .....	56	7.1.4 Modulo-n counters .....	90
5.2.1 8421-BCD / Decimal code converter .....	56	7.1.5 Programmable counters .....	91
5.2.2 8421-BCD / 7-segment code converter ...	58	<b>7.2 Experiments section</b> .....	92
5.2.3 Coding circuits .....	61	7.2.1 Asynchronous up counters .....	92
<b>6. Arithmetic circuits</b> .....	63	7.2.2 Asynchronous down counters .....	94
<b>6.1 Fundamental principles</b> .....	63	7.2.3 Asynchronous reversing counters .....	96
6.1.1 General .....	63	7.2.4 Asynchronous modulo-n counters .....	97
6.1.2 Semi adder .....	63	7.2.5 Synchronous counters .....	99
6.1.3 Full adder .....	64	7.2.6 Programmable counters .....	102
6.1.4 Correction addition for decimal numbers ..	65	<b>8. Register circuits</b> .....	105
6.1.5 Subtractor for dual numbers .....	66	<b>8.1 Fundamental principles</b> .....	105
<b>6.2 Experiments section</b> .....	68	8.1.1 General .....	105
6.2.1 Semi adder .....	68	8.1.2 Shift registers .....	105
6.2.2 Full adder .....	70	8.1.3 Universal shift registers .....	106
6.2.3 Adding circuits for the 8421-BCD code ...	72	<b>8.2 Experiments section</b> .....	107
6.2.4 Semi subtractor .....	77	8.2.1 JK shift registers .....	107
6.2.5 Full subtractor .....	78	8.2.2 Shift registers with parallel data input ...	109
6.2.6 Subtractor for dual numbers .....	81	8.2.3 Serial data transfer .....	111
6.2.7 2-bit parallel multiplication circuit .....	83	<b>9. Multiplex mode</b> .....	115
6.2.8 Arithmetic unit for 4-bit dual numbers ....	85	<b>9.1 Fundamental principles</b> .....	115
<b>7. Counting circuits</b> .....	87	<b>9.2 Experiments section</b> .....	117
<b>7.1 Fundamental principles</b> .....	87		
7.1.1 General .....	87		
7.1.2 Asynchronous counters .....	87		
7.1.3 Synchronous counters .....	88		

---

<b>Solutions section</b> .....	S 1
1. Basic logic circuits .....	S 1
2. Schmitt triggers .....	S 9
3. Bistable multivibrators .....	S 11
4. Monostable multivibrators .....	S 17
5. Code converters, coders .....	S 19
6. Arithmetic circuits .....	S 25
7. Counting circuits .....	S 37
8. Register circuits .....	S 45
9. Multiplex mode .....	S 51
<b>Appendix</b> .....	A 1
1. List of symbols used in the formulae .....	A 1
2. Measuring instruments used .....	A 1
<b>Overhead foils</b> .....	F 1
DIGI BOARD 2 .....	F 1
DIGI MODULE BOARD .....	F 2
Modules .....	F 3

